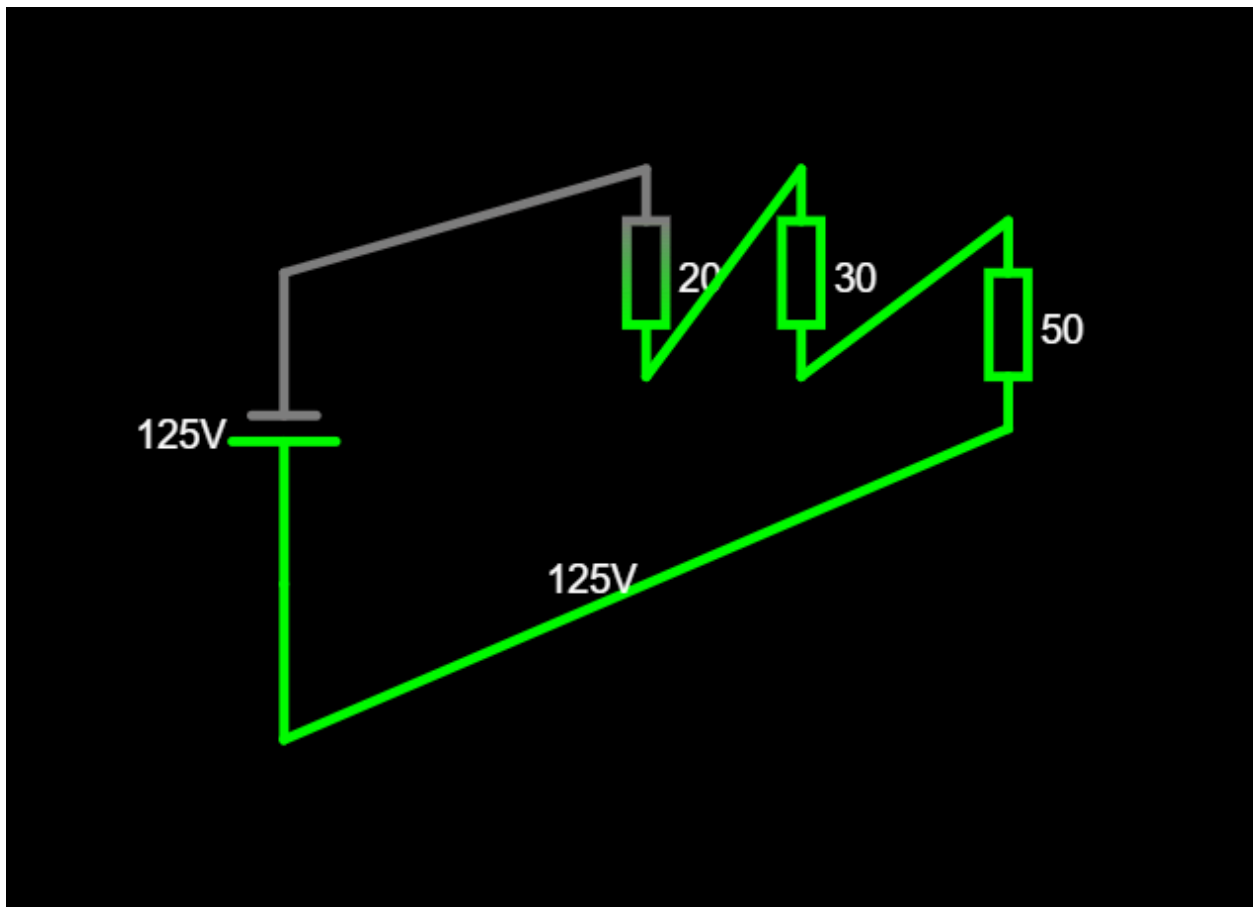


This was simulated in falstad for both circuit a and b

Circuit A



Component Table

Component	Value
Resistor	20 Ohm
Resistor	30 Ohm
Resistor	50 Ohm
2 way DC voltage terminal	125 V

Values along the resistors with their corresponding voltages, voltage drop, current as per our calculations.

50 Ohm resistor




30 Ohm resistor



20 Ohm resistor




Circuit b

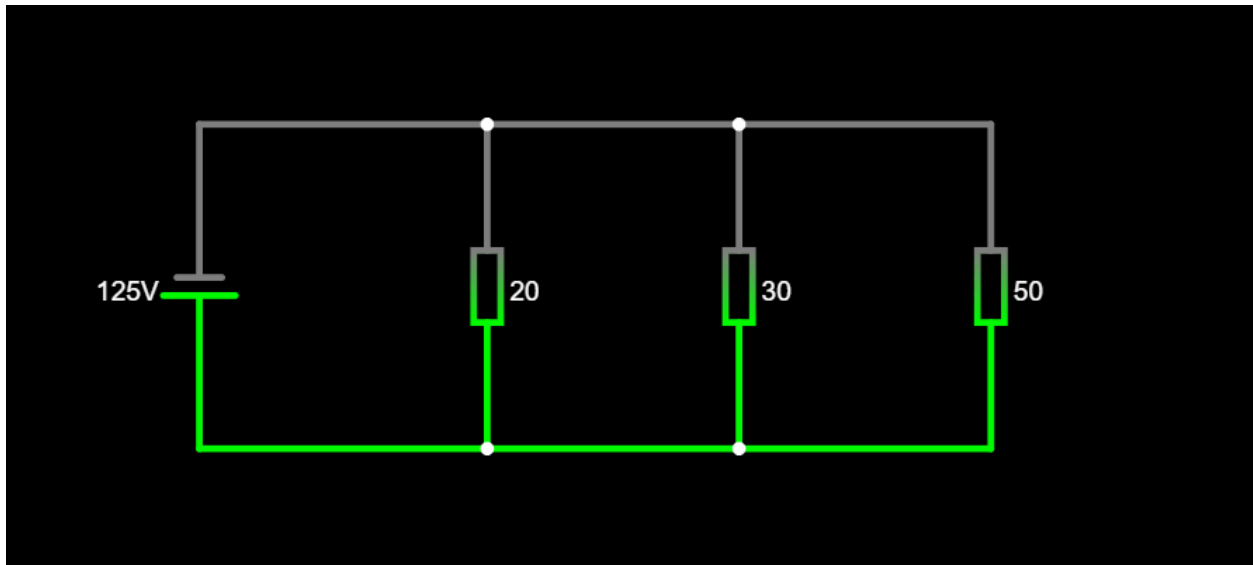


Component table is same as component table for circuit b

Values along the resistors with their corresponding voltages, voltage drop, current as per our calculations.

20 Ohm

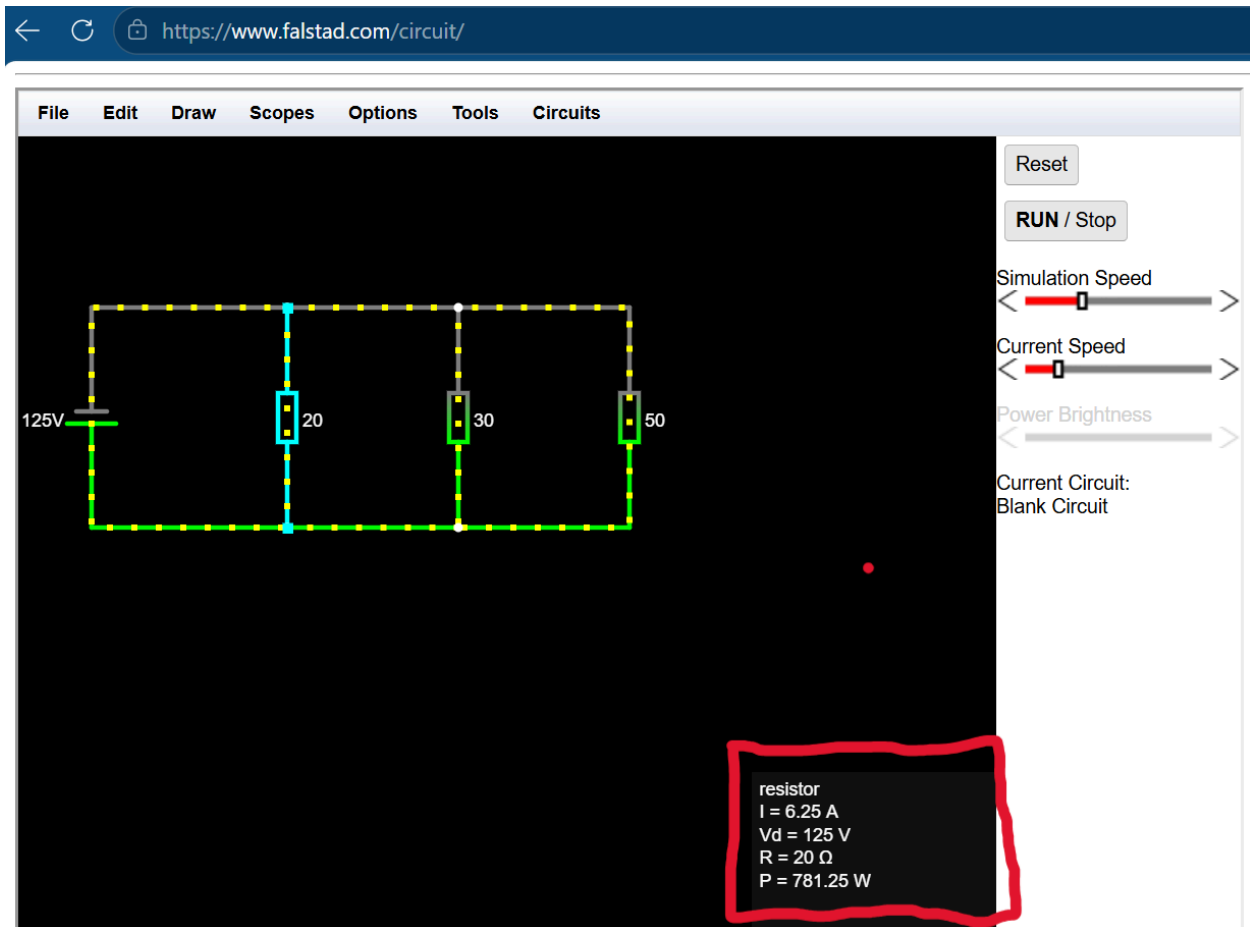

30 Ohm

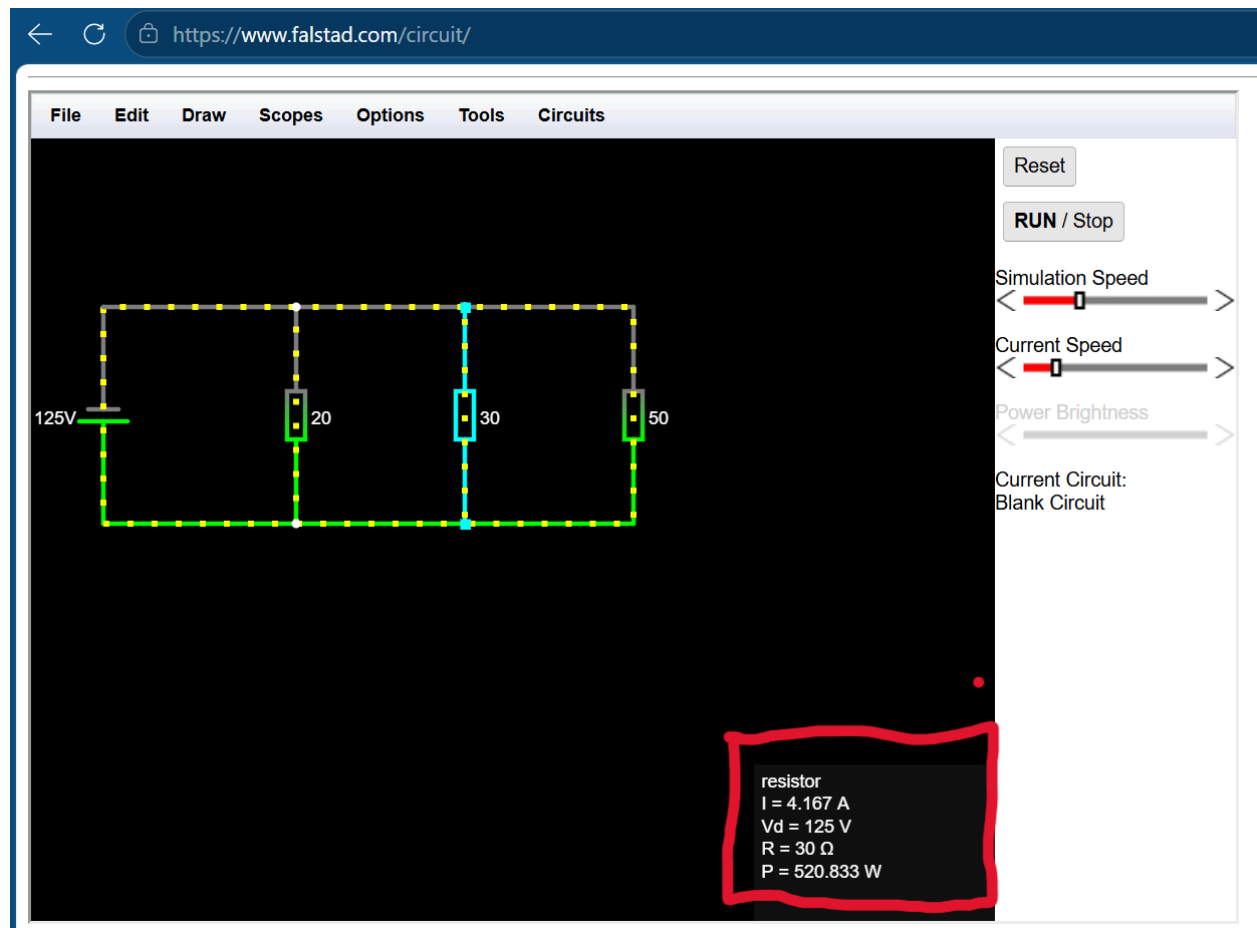

50 Ohm

